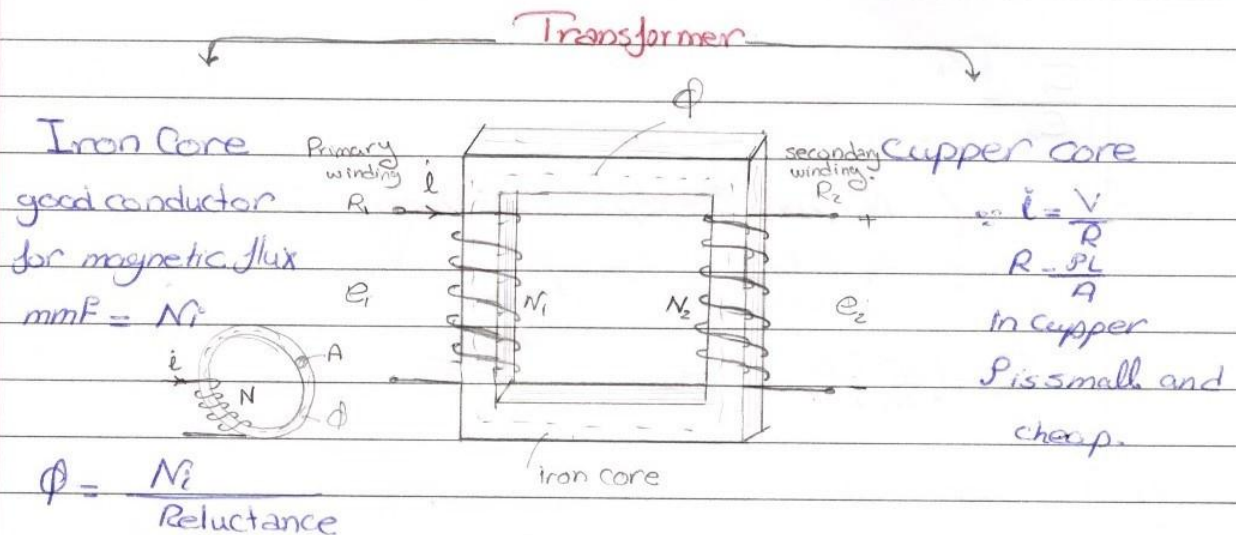


Single phase Transformer.


- To convert power from circuit to another at same frequency "primary ct. to secondary ct."
- Transformer is static Device. & we use it in AC only.



$$R_e = \frac{l}{\mu_0 \mu_r A}$$

μ_r is very high for iron
 $\therefore R_e$ is very small
 $R_{e\downarrow} \rightarrow \Phi \uparrow$

$$e = -N \frac{d\Phi}{dt}$$

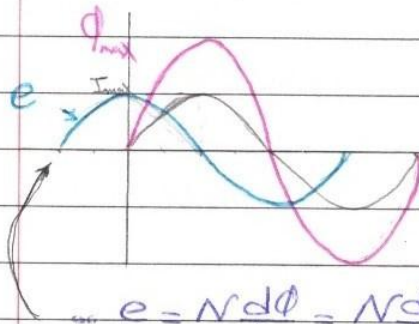

$$i = I_{\max} \sin \omega t$$

$$\Phi = \Phi_{\max} \sin \omega t$$

$$e = -N \frac{d\Phi}{dt} = -N \frac{d(\Phi_{\max} \sin \omega t)}{dt} = N \Phi_{\max} \omega \cos \omega t$$

E_{\max}

$$E_{\max} = N \Phi_{\max} \omega$$

$$E_{\text{rms}} = \frac{N \Phi_{\max} \omega}{\sqrt{2}}$$

$$e_{rms} = \frac{N \Phi_m \omega}{\sqrt{2}} = \frac{2\pi F N \Phi_{max}}{\sqrt{2}} = \sqrt{2} \pi F N \Phi_{max}$$

$$e_{rms} = 4.44 F N \Phi_{max} \quad \#$$

$$E_1 = 4.44 F N_1 \Phi_{max}$$

$$E_2 = 4.44 F N_2 \Phi_{max}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \quad \#$$

✓ $N_1 > N_2$ step down Transf.

✓ $N_1 < N_2$ step up Transf.

$$R_1 = \left(\frac{N_1}{N_2}\right)^2 R_2 \quad \#$$

types of load.	over load	زیاده بار
	full load	در باره است
	half load	نصف بار
	low load	کم بار

Ex: 10 K VA , 250/125 V Transf.

$$\text{Sol: } V_{N1} = 250$$

$$V_{N2} = 125$$

$$10 \times 10^3 = V_1 I_{N1} = V_2 I_{N2}$$

$$= 250 \times I_{N1} = 125 I_{N2}$$


$$I_{N1} = 40 \text{ A}$$

$$I_{N2} = 80 \text{ A}$$


Note: To measure AC \rightarrow RMS

DC \rightarrow average

Equivalent circuit of a transformer.

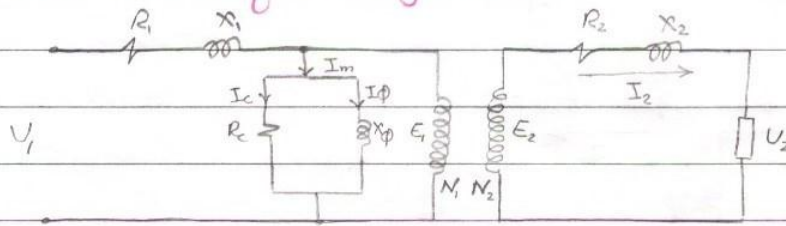


a. Referred to primary side.

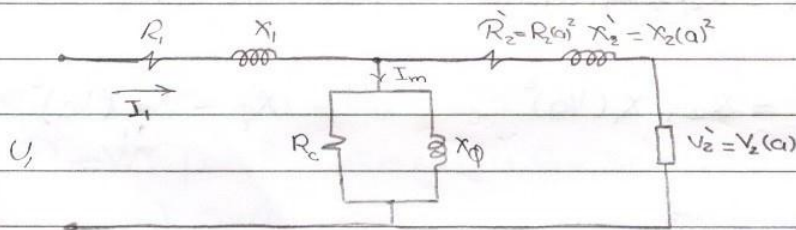

ohm. $\frac{V_2}{a} \approx R_c$

Exact Equivalent Circuit.

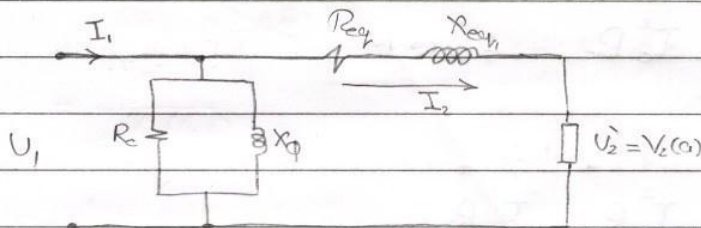

Approximate Equivalent circuit.

$$R_{eq} = R_1 + R_2' \\ = R_1 + R_2(a)^2$$


$$X_{eq} = X_1 + X_2' \\ = X_1 + X_2(a)^2$$

$$V_2' = V_2(a)$$

$$I_2' = I_2 \div a$$

$$\text{where } a = \frac{N_1}{N_2}$$

Referred to secondary side.

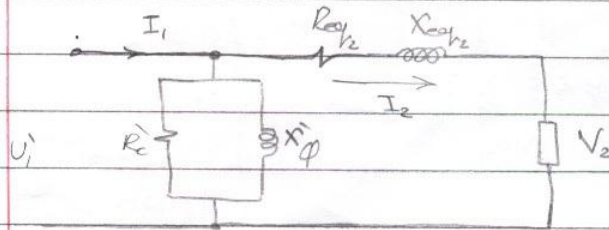

referred jaisi hai
 second. Ji Ky Primary - II
 Given (Circuit) (Circuit)

$$a = \frac{N_1}{N_2}$$

$$V_1' = V_1 \div a$$

$$R_{eqf} = R_2 + R_1' = R_2 + R_1 (V_a)^2$$

$$R_1' = R_1 (V_a)^2$$

$$X_{eqf} = X_2 + X_1' = X_2 + X_1 (V_a)^2$$

$$X_1' = X_1 (V_a)^2$$

Losses

1. Iron losses

$$P_i = I_c^2 R_c \quad \text{"Fixed"} \quad \text{constant}$$

2. Copper losses:-

$$P_{cu} = I_1^2 R_1 + I_2^2 R_2$$

$$= I_1^2 R_{eqf} = I_2^2 R_{eqf2} \quad \text{"Variable"}$$

$$\text{Total loss} = P_i + P_{cu}$$

Power factor:-

1. unity power factor $Z_L = Z_R$


2. lagging power factor: $Z_L = R + jX_L$

3. leading power factor: $Z_L = R - jX_C$

$$PF = \cos \phi$$

exampler.

ex: $\frac{1}{\cos \phi}$

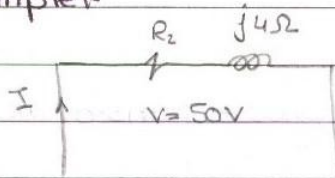

Sol:

$$Z_1 = 3 + j4 = 5 \angle 53.13^\circ$$

$$I = \frac{V}{Z_1} = \frac{50 \angle 0^\circ}{5 \angle 53.13^\circ} = 10 \angle -53.13^\circ$$

$$P.F. = \cos 53.13 = 0.6 \text{ lagging}$$

$$S = V \cdot I = 50 \times 10 = 500 \text{ VA}$$

$$P = V \cdot I \cos \phi = 50 \times 10 \times 0.6 = 300 \text{ W}$$


$$V \cdot I \sin \phi = 50 \times 10 \times 0.8 = 400 \text{ VAR}$$

$$\cos^2 x + \sin^2 x = 1$$

$$\sin x = \sqrt{1 - \cos^2 x}$$

$$= \sqrt{1 - (0.6)^2}$$

$$= 0.8$$

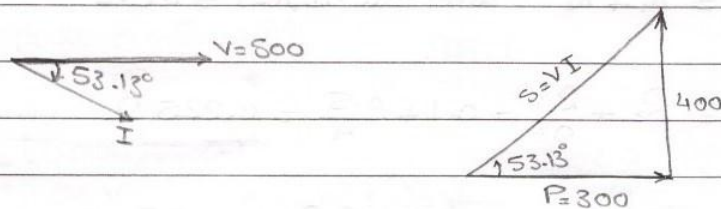

Exampler-

A 5 KVA, 500/250 V single phase transformer has the following parameter.

$$R_1 = 1/2 \Omega \quad X_1 = 0.6 \Omega \quad R_2 = 0.1 \Omega \quad X_2 = 0.15 \Omega$$
$$R_c = 5 K\Omega \quad X_m = 500 \Omega$$

Required-

- 1) R_{eq} & R_{eq_h}
- 2) copper losses at full load & Iron losses
- 3) total losses at half load
- 4) efficiency at full load & half load at 0.8 P.F. lagging.

Sol:-

$$a = \frac{N_1}{N_2} = \frac{500}{250} = 2$$

$$(1) R_{eq_h} = R_1 + R_2' = 1/2 + (0.1)(2)^2 = 0.9 \Omega$$
$$X_{eq_h} = X_1 + X_2' = 0.6 + (0.15)(2)^2 = 1.2 \Omega$$

$$R_{eq_2} = R_2 + \frac{R_1}{a^2} = 0.1 + \frac{0.5}{4} = 0.225 \Omega$$

$$X_{eq_2} = X_2 + \frac{X_1}{a^2} = 0.15 + \frac{0.6}{4} = 0.3 \Omega$$

$$\text{N.B } R_{eq_h} = R_{eq_2}(a)^2$$

(2)

$$5 \text{ KVA} = 5000 = 500 I_{N1} = 250 I_{N2}$$

$$I_{N1} = 10 \text{ A}$$

$$I_{N2} = 20 \text{ A}$$

$$P_{cu \text{ full}} = I_N^2 R_1 + I_N^2 R_2 = (10)^2 (0.5) + (20)^2 (0.1) = 50 + 40 = 90 \text{ W}$$

or

$$P_{cu \text{ full}} = I_{N2}^2 R_{eq_2} = (20)^2 (0.225) = 90 \text{ W}$$

$$P_{\text{half load}} = P_{\text{full load}} \left(\frac{1}{2} \right)^2 = 22.5 \text{ W}$$

$$P_i = I_c^2 R_c$$

$$\text{where } I_c = \frac{V}{R_c} = \frac{500}{5000} = 0.1 \text{ A}$$

$$P_{\text{iron}} = (0.1)^2 \times 5000 = 50 \text{ watt}$$

$$\text{loss at full load} = P_i + P_{cu} = 50 + 90 = 140 \text{ w}$$

at 50% load

$$\text{loss} = 50 + 22.5 = 72.5 \text{ w}$$

iron is a constant loss

Highly efficient

$$\eta = \frac{P_{out} + P_f}{P_{out} + P_f + \text{losses}}$$

$$\eta_{FL} = \frac{5000 \times 0.8}{5000 \times 0.8 + 50 + 90} = 0.966 \%$$

$$= 96.6 \%$$


$$\eta_{HL} = \frac{\frac{1}{2}(5000)(0.8)}{\frac{1}{2}(5000)(0.8) + 50 + 90(0.5)^2} = \frac{2000}{2072.5} = 96.5 \%$$

$$\eta_{x\text{-load}} = \frac{x(\text{kVA})(P.F.)}{x(\text{kVA})(P.F.) + P_{\text{iron}} + P_{cu}(\text{Full load})(x^2)}$$

$$0 < x < 1$$

$$X_m = \sqrt{\frac{P_i}{P_{cu, \text{Full}}}}$$

← X_m is a constant ??

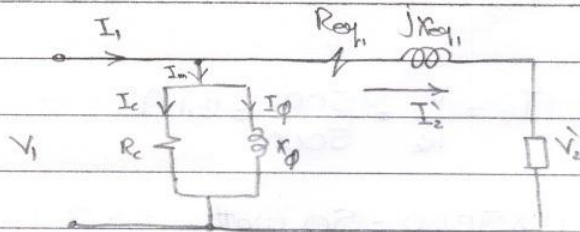

عائدين جانب بقی ال Parameter الی الی R_{cy} و R_c & X_c

Parameters

Iron part

$R_c + X_c$

open circuit test

O.C.T

Copper part

$R_{cy} + X_{cy}$

short circuit test



S.C.T

جانب بدنه ایلی ←


قسم التوازی

(HVS) high voltage side → Primary

یعنی عند (HVS) Secondary

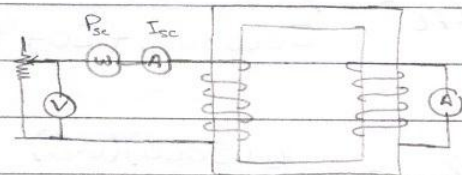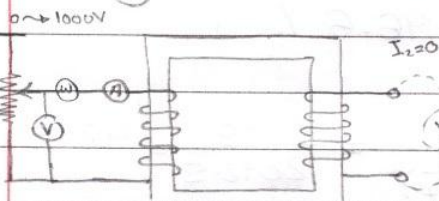

V_1	I_1	P_1	V_2
100			50
200			
300			250

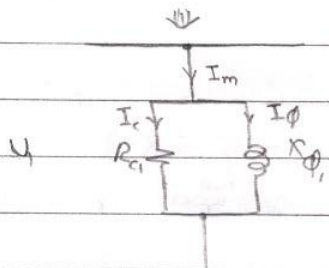


sec. جانب سوا O.C.T (HVS):

open 500V, 1A, 120W

بدنه ایلی (HVS) بدنه ایلی

Power transformer


secondary is open

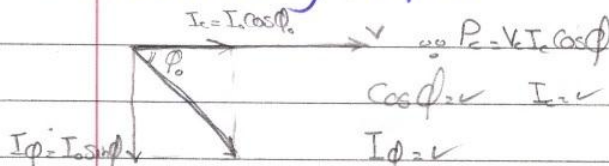

بدنه ایلی ال بدنه ایلی Primary لانه بدنه ایلی ال بدنه ایلی

الجهد 250 بد 500 و بدنه ایلی ال بدنه ایلی Primary

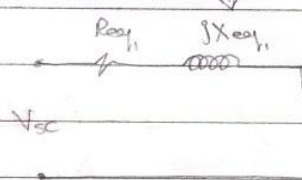حرفه بدنه ایلی بدنه ایلی ال بدنه ایلی sec.




$$P_{sc} = I_{sc}^2 R_{cy}$$

$$R_{cy} = \frac{P_{sc}}{I_{sc}^2}$$

$$V_{sc} = I_{sc} Z_{cy}$$

$$X_{cy} = \sqrt{Z_{cy}^2 - R_{cy}^2}$$

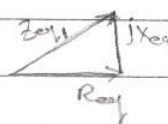

هذا أهل الدائرة بدنه ایلی ال iron لانه ال 500V Volt

كان هاتفي تيار 1A وفي الدائرة ال الجهد ال 50V

يعني التيار ال 1A فهدن أهل الدائرة

Example: 10 KVA, 500/250 V, single phase transformer has a following test data:-

open circuit test (O.C.T) (H.V.S), 500V, 1A, 200 watt

short circuit test (S.C.T) (L.V.S), 25V, 40A, 600 watt

(1) obtain the parameter of this transformer referred to primary & referred to secondary side.


(2) obtain the max. efficiency at 0.8 P.f. lagging.

Soln-

(9)

O.C.T (H.V.S)

500V, 1A, 200 watt

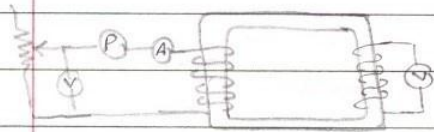

$$P_o = V_o I_o \cos \phi$$

$$\cos \phi = \frac{200}{(500)(1)} = 0.4$$

$$\sin \phi = 0.96$$

$$I_c = I_o \cos \phi = 0.4 \text{ A}$$

$$I_\phi = I_o \sin \phi = 0.96 \text{ A}$$

$$R_o = \frac{V_o}{I_c} = \frac{500}{0.4} = 1250 \Omega$$


$$X_\phi = \frac{V_o}{I_\phi} = \frac{500}{0.96} = 545.5 \Omega$$

$$R_e = \frac{R_o}{a^2} = \frac{1250}{4} = 312.5 \Omega$$

$$X_\phi = \frac{X_\phi}{a^2} = \frac{545.5}{4} = 136.4 \Omega$$

S.C.T (L.V.S)

25V, 40A, 600 watt

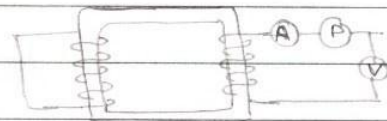

$$P_{sc} = I_{sc}^2 R_{eq2}$$

$$R_{eq2} = \frac{600}{(40)^2} = 0.375 \Omega$$


$$V_{sc} = I_{sc} Z$$

$$Z = \frac{V_{sc}}{I_{sc}} = \frac{25}{40} = 0.625 \Omega$$

$$X_{eq2} = \sqrt{Z^2 - R_{eq2}^2} = 0.5 \Omega$$

$$R_{eq1} = R_{eq2} a^2 = 4 \times 0.375 = 1.5 \Omega$$

$$X_{eq1} = X_{eq2} a^2 = 2 \Omega$$

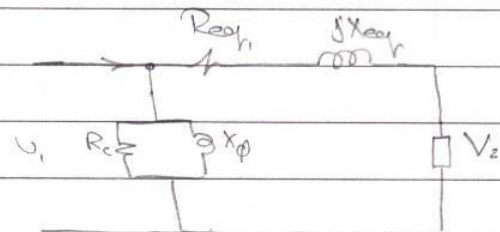

جواب: 1) X_{ϕ} و R الی (H.V.S) و X_{ϕ} و R الی (L.V.S) کے لئے
Primary-referred R و X_{ϕ} الی (H.V.S) کے لئے (referred to primary)
referred to secondary R و X_{ϕ} الی (L.V.S) کے لئے

(b)

$P_{in} = 200 \text{ W}$ "open ct."

or $I_c^2 R_c = 200W$

$$P_{cu(FL)} = I_{N_1}^2 R_{eq1} = I_{N_2}^2 R_{eq2}$$

$$= (20)^2 (1.5) = (40)^2 (0.375) = 600 \text{ W}$$


Short circuit test (Circuit) of a transformer.

∴ The change in the secondary voltage from no load to full load for the same primary voltage

Voltage Regulation

* The voltage regulation is like the figure of merit of a transformer.

Ideal transformer V.R = zero.

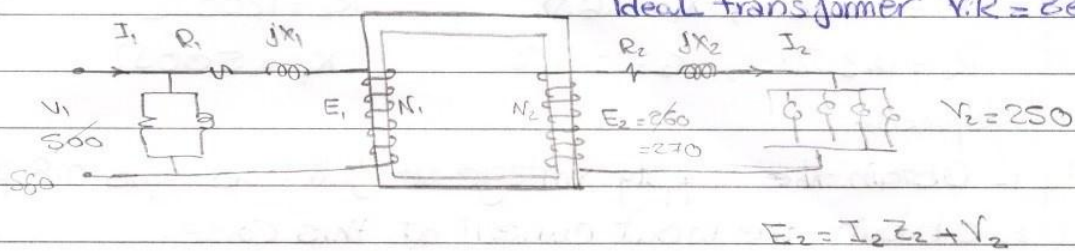


$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = a$$

$$* V.R = \frac{V_1 - V_2'}{V_2} = \frac{580 - 500}{500} = \frac{80}{500} = 16\%$$

$$V.R = V_1 - V_2$$
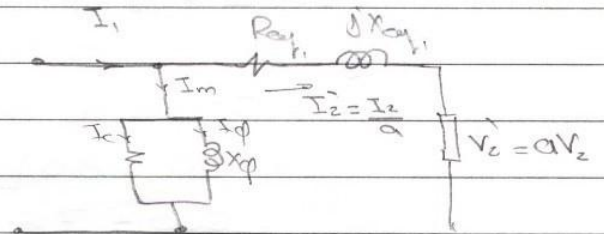
$$V.R\% = \frac{V_1 - V_2'}{V_2} \times 100 =$$




$$I_1 = I_2 \angle \phi_2 + \frac{V_1}{R_0} - j \frac{V_1}{X_0}$$

$$= a \angle \phi_2 = \sqrt{a^2 + b^2} \angle \tan^{-1} \frac{b}{a}$$

$$V_1 = V_2' \angle 0 + I_2' \angle \phi_2 Z_{eq1} \angle \theta$$

$$= A + jB$$

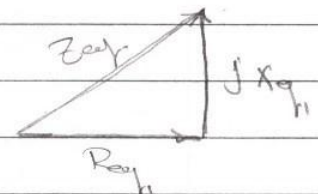

$$V_1 = \sqrt{A^2 + B^2} \angle \tan^{-1} B/A = \phi_1$$

$$\text{where } |Z_{eq}| = \sqrt{R_{eq}^2 + X_{eq}^2} \angle \tan^{-1} X_{eq}/R_{eq}$$

$$P_m = V_1 I_1 \cos \phi_1$$

$$\text{where } \phi_1 = \alpha + \beta$$

$$P_{out} = V_2 I_2 \cos \phi_2$$

ex8-

Example: 10 kVA, 500/250 V, single phase transformer has the following parameter.

$$R_1 = 1.2 \Omega, X_1 = 1.6 \Omega \quad R_c = 1200 \Omega$$

$$R_2 = 0.3 \Omega, X_2 = 0.4 \Omega \quad X_\phi = 500 \Omega$$


Required:-

- (V₁) 1. Obtain the supply voltage at full load and 0.8 p.f lagging
- (I₁) 2. Obtain the input current at this case.
- $\frac{(V_1 - V_2)}{V_2}$ 3. Obtain the voltage regulation.

Sol:-

$$R_{eq} = 1.2 + 0.3(2) = 2.4 \Omega$$

$$X_{eq} = 1.6 + (0.4)(4) = 3.2 \Omega$$

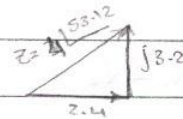

$$V_1 = V_2 I_2 + I_2 Z$$

$$\frac{(250)(40)}{2} \rightarrow 500 I_2 + (20 \angle -36.87^\circ)(4 \angle 53.13^\circ)$$

$$= 500 I_2 + 80 \angle 16.26^\circ$$

$$= 500 + 80 [0.96 + j0.28]$$

$$= 500 + 76.8 + j22.4$$

$$= 576.8 + j22.4 = 577.23 \angle 2.22^\circ$$

$$V.R = V_1 - V_2 = 77.23 V = \frac{77.23}{500} \times 100 = 15.44 \%$$

$$I_1 = I_2 + I_c + I_\phi$$

$$= 20 \angle -36.87^\circ + \frac{577.23}{1200} = j \frac{577.23}{500}$$

$$= 16 \angle -j12 + 0.48 - j1.175$$

$$\approx 16.48 - j13.15 = 21.08 \angle -38.58^\circ$$

$$P_i = V_1 I_1 \cos \phi = 577.23 \times 21.08 \times \cos(38.58 + 2.22) \times 0.8$$

$$= 9211.1 W$$

$$P_{out} = V_2 I_2 \cos \phi = 250 \times 40 \times 0.8 = 8000 \text{ watt}$$




Chapter II

Three phase Induction Motors.


Stator + Rotor

(wound Rotor)
high power


(squirrel cage Rotor)
low power

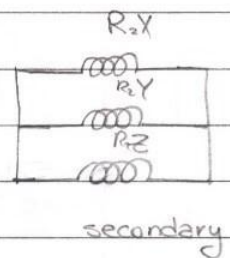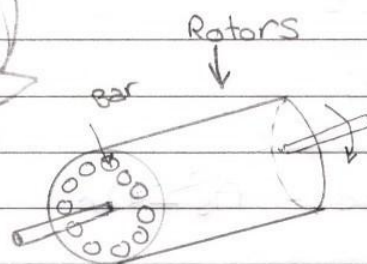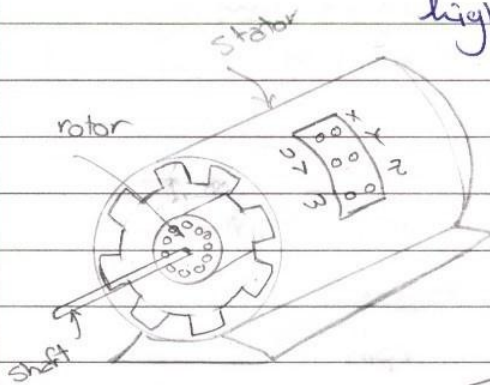

سجّل میاد کبیر
squirrel cage

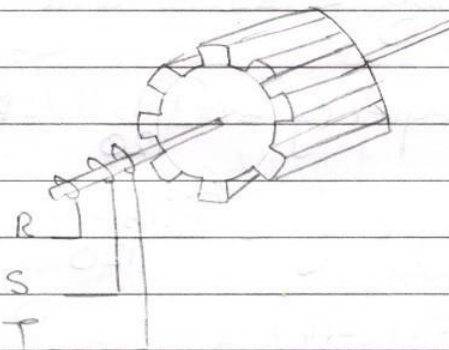


Star

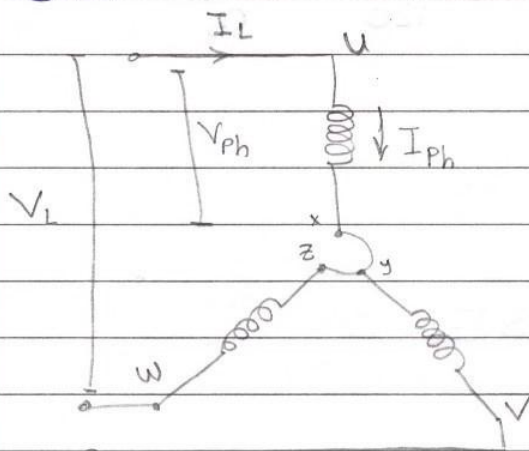

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

Delta

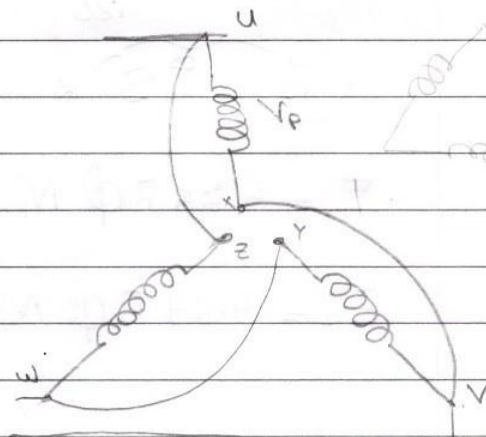

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$\text{Let slot } (S) = 12$$


$$\text{Poles } (P) = 2$$

$$\text{Phases } (m) = 3$$

$$* n_s : \text{Synchronous speed} = \frac{120f}{P} \text{ rpm}$$

$$= \frac{120 \times 50}{2} = 3000 \text{ rpm}$$

$$\text{emf} = N \frac{d\phi}{dt}$$

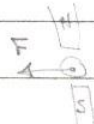

$$F = Bli$$

$$* \text{Slip speed} = n_s - n_r \text{ rpm}$$

$$* S = \frac{n_s - n_r}{n_s} \quad 0 \leq S \leq 1$$

$$\text{at starting } S = 1 \text{ and } n_r = 0$$

$$* \text{Stator frequency} = \frac{P n_s}{120} = f_1$$

$$* \text{Rotor frequency} = \frac{P(n_s - n_r)}{120} = f_2$$

$$\therefore f_2 = \frac{P(n_s - n_r)}{120} \times \frac{n_s}{n_s} = \frac{P n_s}{120} \cdot \frac{n_s - n_r}{n_s}$$

$$f_2 = f_1 S \quad *$$


$$E_1 = 4.44 f \phi N_{ph}$$

$$E_2 = 4.44 f \phi N_{ph} \approx S E_1$$

Equivalent Circuit

$$I_2 = \frac{SE_2}{R_2 + jSX_2}$$


$$= \frac{E_2}{\frac{R_2}{S} + jX_2}$$

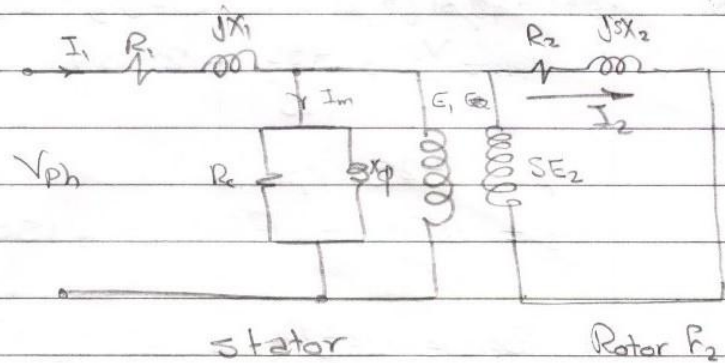

$$\frac{R_2}{S} = R_2 + \frac{R_2(1-S)}{S}$$

$$= R_2 + R_m$$

↓ resistance due to load.

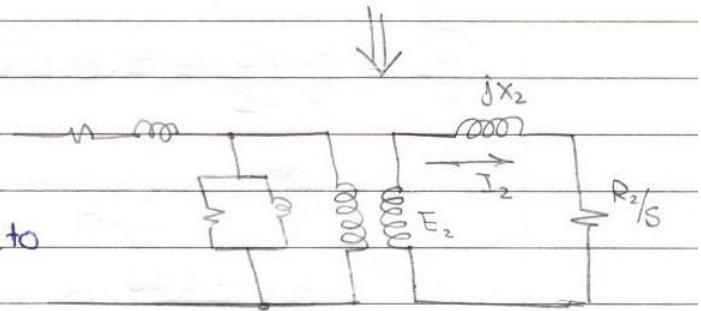

Examples-



A 433V star connection four Pole 50Hz, 1425 rpm

Three phase induction motor has the following Parameter

$R_1 = 0.1\Omega$, $X_1 = 0.3\Omega$, $R_2' = 0.115$, $X_2' = 0.4\Omega$, $R_c = 125\Omega$
 $X_\phi = 50\Omega$, obtain

- 1- The slip at full load
- 2- The input current and input power factor.
- 3- The full load efficiency if the fractional losses = 2.3
- 4- The starting Torque in newton meter.

all 1.5 and 2.3 and 4.3

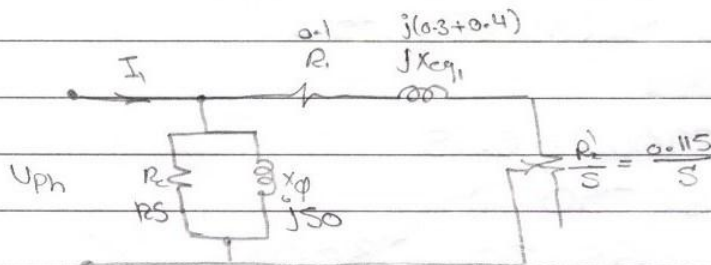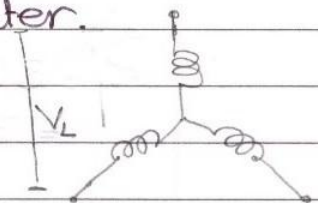

* لوصل المكنر الى P_1 في آلة المحرك ب ∞

* دليلاً ان Volt التي يتدفق هو V_L ولولاً Δ صيفي المكنر هو P_{ph}

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{433}{\sqrt{3}} = 250V$$

$$n_f = 1425 \text{ rpm}$$

$$n_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$(a) S_{FL} = \frac{n_s - n_f}{n_s} = \frac{1500 - 1425}{1500} = 0.05 \quad P_u = 5\%$$

$$\frac{R_2'}{S} = \frac{0.115}{0.05} = 2.3 \Omega$$

$$(b) I_2' = \frac{V_{ph}}{(0.1 + 2.3) + j0.7} = \frac{250 \angle 0}{2.4 + j0.7} = \frac{250 \angle 0}{2.2 \angle 16.26} = 100 \angle -16.26 \text{ A} = 96 - j28$$


$$I_m = I_c + I_\phi = \frac{250}{125} - j \frac{250}{50} = 2 - j5$$

$$I_1 = I_m + I_2' = 98 - j33 = 103.4 \angle -18.6 \text{ A}$$

دليلاً $\cos \phi$ هو

I_1 هو
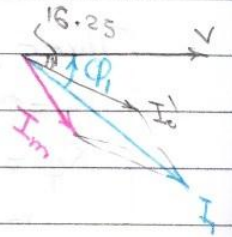
$$PF = \cos \phi = \cos 18.6 = 0.9477 \text{ lagging}$$



(c)

$$P_{in} = P_{cu} + P_{core} + P_g = 3I_1^2 R_1' + 3I_2'^2 \frac{R_2'}{S}$$

$$P_{in} = 3(250)(103.4)(0.9477) = 73495 \text{ W}$$

$$P_{cu} = 3I_1^2 R_1' = 3(103.4)^2(0.1) = 3180 \text{ W}$$

$$P_{core} = 3I_2'^2 \frac{R_2'}{S} = 3(100)^2(2.3) = 69000 \text{ W}$$

$$P_g = P_{in} - P_{cu} - P_{core} = 73495 - 3180 - 69000 = 1315 \text{ W}$$

$$P_g = 3I_2'^2 \frac{R_2'}{S} = 3(100)^2(2.3) = 69000 \text{ W}$$

$$P_m = P_g(1 - S) = 69000 \times 0.95 = 65550 \text{ W}$$

$$P_{out} = P_m - P_f = 65550 - 2300 = 63250 \text{ W}$$

$$P_{out}|_{hp} = \frac{63250}{746} = 84.7 \text{ hp}$$

hp = W في الـ 746
746

$$\eta = \frac{63250}{73495} = 86\%$$

(d)

$$T_{fl} = \frac{P_{ef}}{\omega_s} = \frac{69000}{2\pi \times \frac{1500}{60}} = \frac{69000}{50\pi} = 439.5 \text{ N.m}$$

على L في الجيب الـ Torque (في)
- الـ S في الـ L في الجيب الـ Torque (في)

→ Starting torque at $s=1 \Rightarrow T_{st}$ starting torq.

$$I_2' = \frac{250}{(0.112 + j0.7)} = 341.4$$

التيار عند الـ start (تيار)

$$P_g = 3(341.4)^2 0.115 = 40212 \text{ W}$$

$$T_{st} = \frac{P_{gst}}{\omega_s} = \frac{40212}{50\pi} = 256 \text{ N.m}$$

$$\text{ratio of } T_{st} \text{ to } T_{fl} = \frac{256}{439.5} = 0.58 = 58\%$$

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

$$n_s = \frac{120f}{P} \text{ rpm}$$

$$S = \frac{n_s - n_r}{n_s} \text{ pu "Per unit"} \quad n_s > n_r \text{ أو } \frac{n_s}{n_r} > 1$$

* at starting ($n_r = 0$) $\Rightarrow S = 1$

* at no load $n_r \rightarrow n_s \Rightarrow s \rightarrow 0 \Rightarrow 0 < s < 1$

$$S_{FL} = [0.03 \rightarrow 0.06]$$

$$\frac{R_2}{S} \rightarrow R_2$$

خاتمه ار S / فہم اقل من 1

$$\frac{R_2}{S} = R_2 + R_m$$


$$\text{Or } \frac{R_2}{S} = R_2 + \frac{R_2(1-S)}{S}$$

علت دی کوه لاله انا اصل عیسی

R_2 (دفعه) ثابتہ والی Load


مسافر فخری R_m
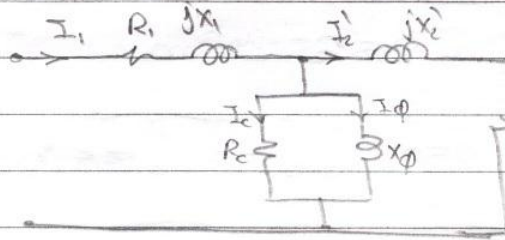
$$\frac{R_2}{S} = R_2 + \frac{R_2(1-S)}{S}$$



Exact E. Circuit

* \rightarrow Approximate Elec. Circuit

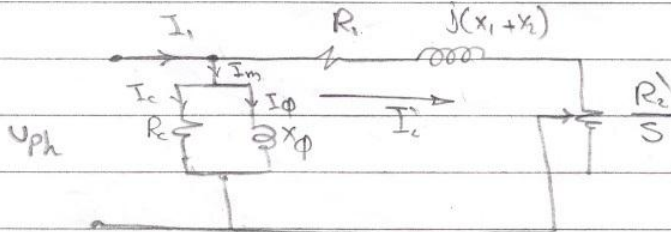

$$R_{eq} = R_1 + R_2$$

$P_1 = P_2 = 5$


$$I_m = I_c + I_\phi = \frac{V_{ph}}{R_c} - j \frac{V_{ph}}{X_\phi}$$

$$I_2' = \frac{V_{ph} \frac{L_c}{s}}{(R_1 + \frac{R_2'}{s}) + jX_{eq}} = \frac{V_{ph} \frac{L_c}{s}}{\sqrt{(R_1 + \frac{R_2'}{s})^2 + X_{eq}^2}} \angle -\tan^{-1} \frac{X_{eq}}{R_1 + \frac{R_2'}{s}}$$

$$I_1 = I_m + I_2' = |I_1| \angle -\phi_1$$

$$P_{in} = 3 V_{ph} I_1 \cos \phi_1$$

3 phase $\sim 1 \angle \phi_1$

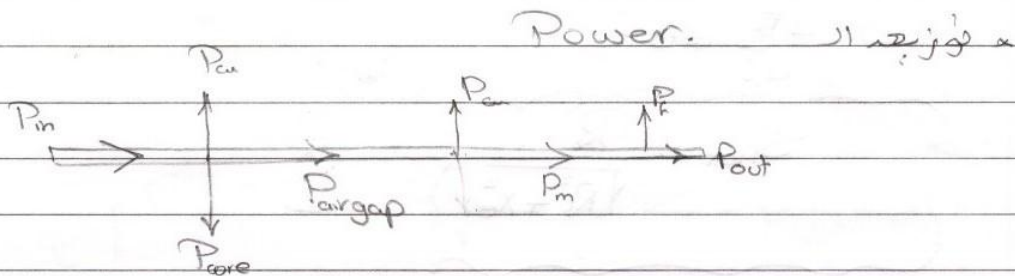

$$P_{in} = 3 V_{ph} I_1 \cos \phi_1$$

three phase

stator losses

$$P_{cu} = 3 I_1^2 R_1$$

$$+ P_{core} = 3 I_c^2 R_c$$

Air gap power

$$P_g = T \omega_s$$

$$= 3 I_2'^2 \frac{R_2'}{s}$$

$$P_{core} = 3 I_2'^2 R_c'$$

$$= s P_g$$

$$P_m = 3 I_2'^2 R_m$$

$$= P_g (1-s)$$

Notes: losses of iron in rotor is very small

$$\omega_m = \frac{2\pi n_r}{60} *$$

$$P_{elec} = V \cdot I$$

$$P_{fr}$$


Given

$$P_{out}$$

$$= T_{sh} \omega$$

$$\omega_s = \frac{2\pi n_s}{60} *$$

$$P_{Mech} = T \cdot \omega$$

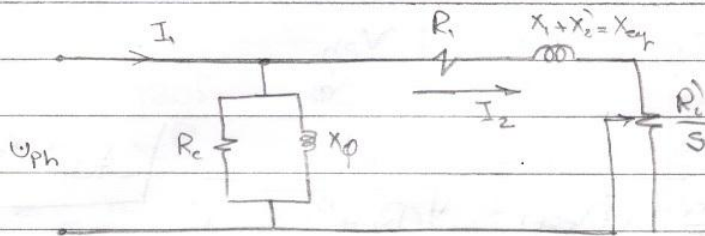

$$T_d = \frac{P_g}{\omega_s} = \frac{3 I_2^2 R_2/s}{\omega_s} = \frac{3 R_2'}{\omega_s S} I_2^2$$

$$= \frac{3 R_2'}{\omega_s S} \frac{V_{ph}^2}{(R_1 + \frac{R_2'}{S})^2 + X_{eq}^2}$$

To Get Max. \$S\$

$$\frac{dT_d}{dS} = 0$$

$$\infty S_{max} = \frac{R_2'}{\sqrt{R_1^2 + X_{eq}^2}} \quad \# \quad \text{ber}$$

$$T_{max} = \frac{3 V_{ph}^2}{3 \omega_s [R_1 + \sqrt{R_1^2 + X_{eq}^2}]}$$

\$\rightarrow R_2\$ less \$\downarrow\$

* assume \$R_1=0\$ "stator"

$$\infty T_d = \frac{3}{\omega_s} \frac{V_{ph}^2}{(\frac{R_2'}{S})^2 + X_{eq}^2} \frac{R_2'}{S} = K S$$


$$S_{max} = \frac{R_2'}{X_{eq}} \quad \#$$

$$T_{max} = \frac{3 V_{ph}^2}{2 \omega_s X_{eq}} \quad \#$$

$$\frac{T}{T_{max}} = \frac{2 \frac{R_2'}{S} X_{eq}}{(\frac{R_2'}{S})^2 + (X_{eq})^2} = \frac{2}{\frac{R_2'}{S X_{eq}} + \frac{S X_{eq}}{R_2'}} = \frac{2}{\frac{S_{max}}{S} + \frac{S}{S_{max}}}$$

$$\frac{T}{T_{max}} = \frac{2 T_{max}}{\frac{S_{max}}{S} + \frac{S}{S_{max}}}$$

Given \$T_{max}\$, \$S_{max}\$

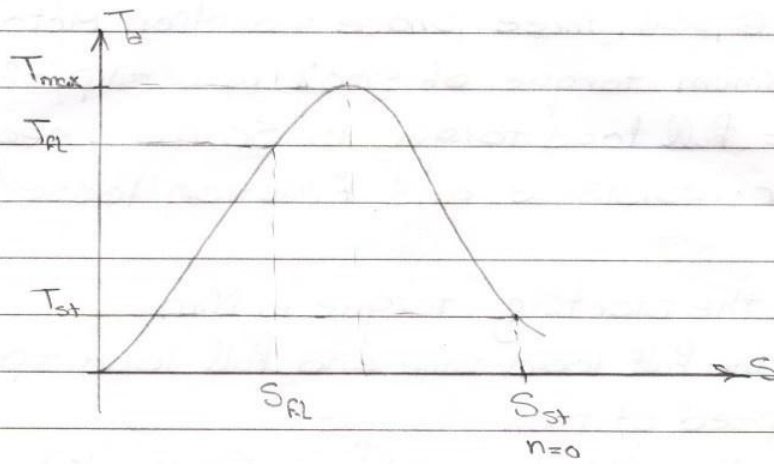

(TIS curve)


$$S = \frac{n_s - n}{n_s}$$

$$S n_s = n_s - n$$

$$n = n_s - S n_s$$

$$n = n_s (1 - S)$$

کل n از n باقی S بنزید

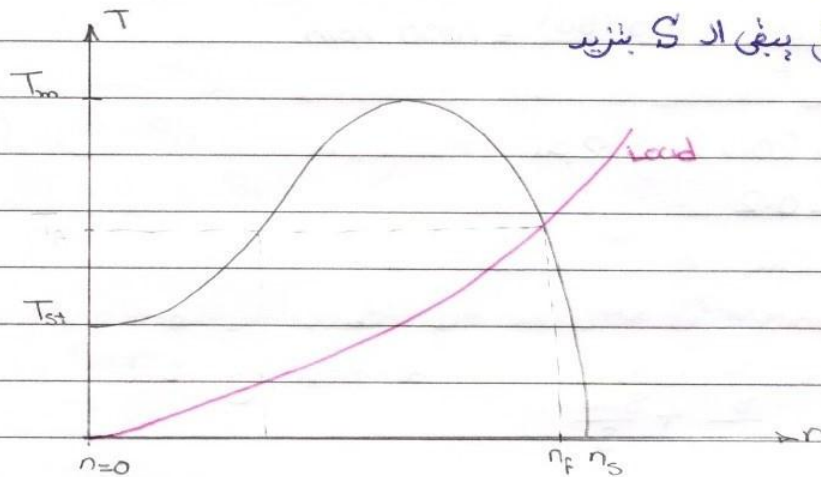

(TIn curve)

$s=1$

$s=0$

افزایش S

Example 8.

A 50 Hz, 6 pole, three phase induction Motor has a maximum torque of 200% at a slip of 0.2 if the Full load torque is 50 N.m. neglect the stator resistance and Friction losses

1. Obtain the starting torque in N.m
2. Obtain the Full load slip and Full load speed
3. The speed at Max. torque
4. Obtain the added resistance to the rotor to obtain the max torque at starting at the same torque
5. Obtain the Radd to change the speed at full load to 900 R.P.M

Sol:

$$n_s = \frac{120f}{p} = \frac{120(50)}{6} = 1000 \text{ rpm}$$

$$T_{max} = 200\% = 2 p.u.$$

$$s_{max} = 0.2$$

$$T_{FL} = 50 \text{ N.m}$$

$$(a) \quad T_s = \frac{2 T_{max}}{\frac{s}{s_{max}} + \frac{s_{max}}{s}} \quad \text{at starting } s=1$$

$$T_s = \frac{2(2)}{\frac{1}{0.2} + \frac{0.2}{1}} = \frac{4}{5.2} = 0.77 \text{ P.u.}$$

(b) Full load at s_f

$$T_{FL} = \frac{2 T_{max}}{\frac{s_f}{s_{max}} + \frac{s_{max}}{s_f}}$$

Torque in full load is 1 P.u.

$$1 = \frac{2(2)}{\frac{s_f}{0.2} + \frac{0.2}{s_f}} \Rightarrow \frac{s_f}{0.2} + \frac{0.2}{s_f} = 4$$

$$S_f^2 + 0.04 = 0.8 S_f$$

$$S_f^2 - 0.8 S_f + 0.04 = 0$$

$$S_f = 0.746$$

refused

$$S_f = 0.053$$

Accept

$S_{max} > S_f$ (من أجل S_f الـ S_{max})

$$S_{max} > S_f$$

$$\therefore S_f = 0.053 \quad P_u = 5.3 \%$$

$$n_f = n_s(1 - S_f) = 1000(1 - 0.053) = 947 \text{ rpm}$$

$$(6) \quad n_{max} = n_s(1 - S_m)$$

$$= 1000(1 - 0.2) = 800 \text{ rpm.}$$

$$R_{add} = \frac{S_2 - S_1}{S_1} R_2$$

في

(d) to obtain max. torque at the start of the same torque
(S1) (S2)

$$\therefore S_1 = S_{max}$$

$$S_2 = S_{st} = 1$$

$$\therefore R_{add} = \frac{1 - 0.2}{0.2} R_2 = 4 R_2$$

(e) to change speed at full load to 900 rpm

$$S = \frac{n_s - n_r}{n_s}$$

$$S_{f1} = 0.053 \text{ calculated in (b)}$$


$$S_{900} = \frac{n_s - 900}{n_s}$$

$$S_{900} = \frac{1000 - 900}{1000} = 0.1$$

$$\therefore R_{add} = \frac{0.1 - 0.053}{0.053} R_2 = 0.88 R_2 \approx R_2$$

Note 8-

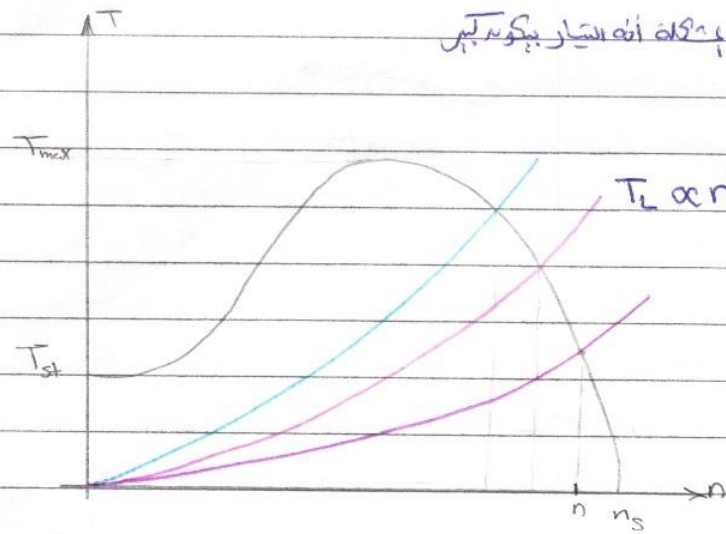پہلے ہی ای Motor کی آکر
اد T و n کے ساتھ کہہ سکتے ہیں




کل LL آؤد الخل پر سے نفل



* Speed control of induction Motor.

- 1- Pole changing " squirrel case "
- 2- Line Frequency control
- 3- line Voltage control
- 4- Rotor resistance control " wound Rotor "


1- Pole changing.

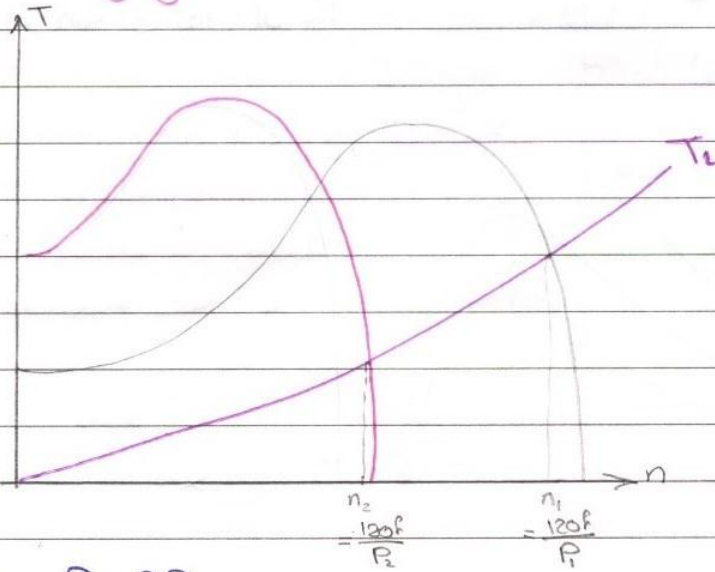

لفظ اللفظ بـ
connection

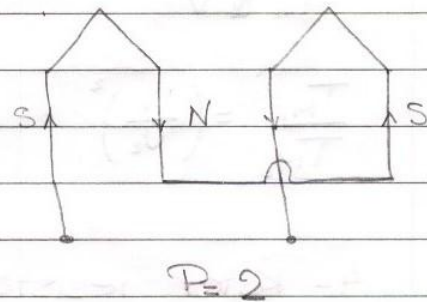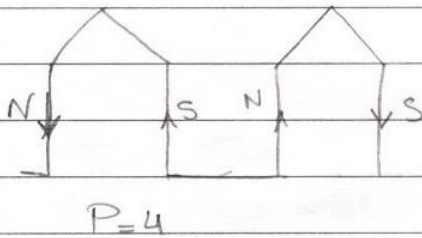

2. Frequency control

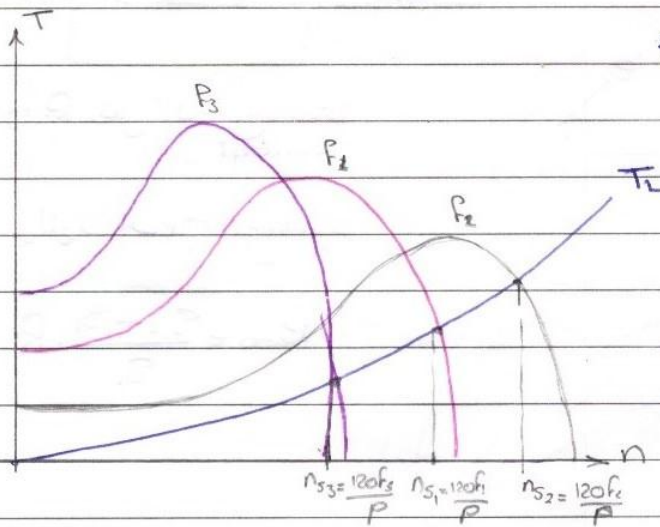


$$T_{max} = \frac{3V_{ph}^2}{2\omega_s X_{eq}} \propto \left(\frac{V}{f}\right)^2$$

$$\frac{T_{m1}}{T_{m2}} = \left(\frac{f_2}{f_1}\right)^2$$

3] line voltage control

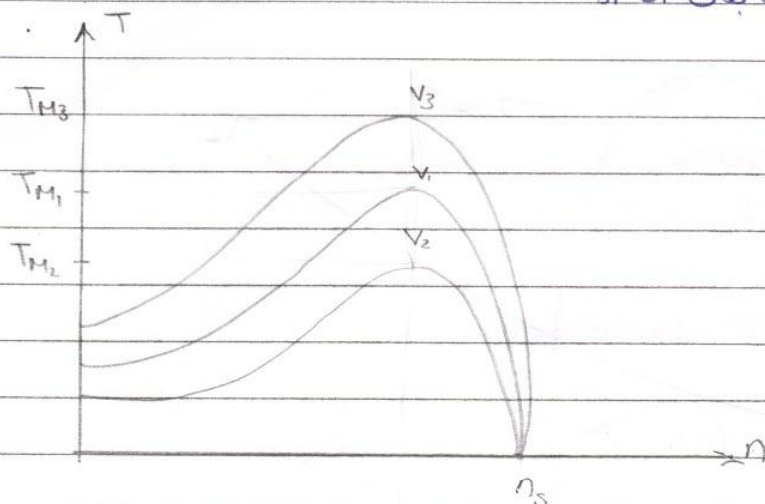مقدار الجهد الـ DC
وتحكم في عزم الـ T_{st}




$$V_3 > V_1 > V_2$$

$$T_m \propto V^2$$


$$\frac{T_{m1}}{T_{m2}} = \left(\frac{V_1}{V_2}\right)^2$$

4- Rotor resistance control

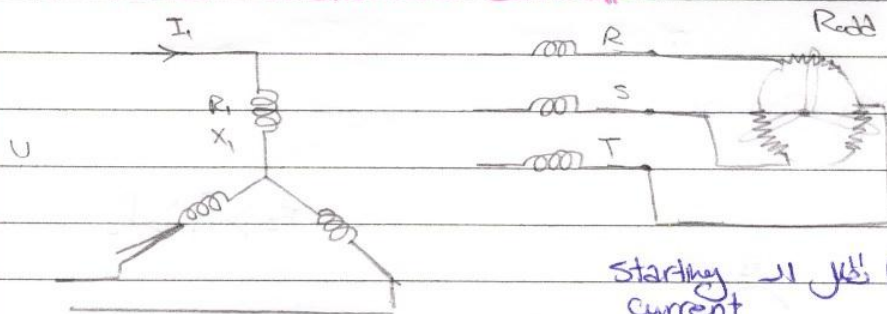

Starting current الـ R_{add}

ولتكون الـ starting torque

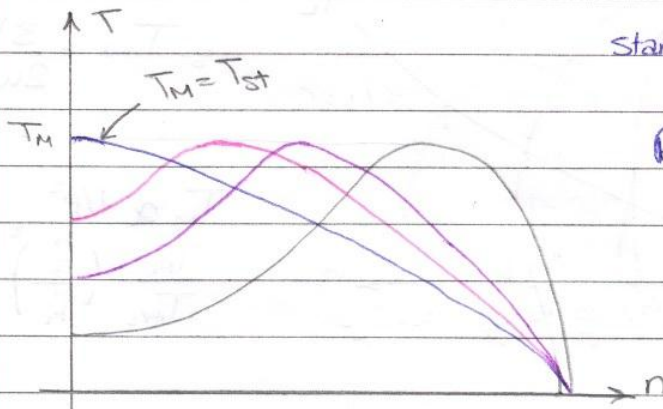

$$R_{add} = \frac{s_2 - s_1}{s_1} \cdot R_2$$

A 50 hp power, 3 phase, 440 V, 4 pole, 60 Hz wound rotor induction motor developed its rated torque at a speed of 1746 rpm. The max Torque is 200% and the rotor resistance = 0.152, neglect rotational losses and the stator resistance.

- Calc. 1- The slip at Max torque & the speed.
 2- The starting torque in N.m
 3- Radd to produce a Max Torque at starting.

Sol: $P = 4$ $f = 120$

$$n_s = \frac{120f}{P} = \frac{120(60)}{4} = 1800 \text{ rpm}$$

$$n_f = 1746 \text{ rpm}$$

$$S_f = \frac{n_s - n_f}{n_s} = \frac{1800 - 1746}{1800} = 0.03 \text{ pu} = 3\%$$

$$(a) \quad T_f = \frac{2T_{max}}{\frac{S_{max}}{S_f} + \frac{S_f}{S_{max}}} \quad \text{eg } T_{max} = 200\% = 2 P_u$$

$$1 = \frac{2(2)}{\frac{S_{max}}{0.03} + \frac{0.03}{S_{max}}}$$

$$\frac{S_{max}}{0.03} + \frac{0.03}{S_{max}} = 4$$

$$S_{max}^2 + 9 \times 10^{-4} = 0.12 S_{max}$$

$$S_{max}^2 - 0.12 S_{max} + 9 \times 10^{-4} = 0$$

$$S_{max} = 0.112$$

$$S_{max} = 0.008$$

Accept

refused

because S_{max} must greater than S_{fl}

$$n_{max} = n_s(1 - S) = 1800(1 - 0.112) = 1598.4 \text{ rpm}$$

$$(b) T_{st} = \frac{2 T_{max}}{\frac{S_{max}}{S_{st}} + \frac{S_{st}}{S_{max}}}$$

$$= \frac{4}{\frac{0.112}{1} + \frac{1}{0.112}} = 0.4425 P_u$$

بہاؤ کی مقدار N.m

دیا گیا ہے

reference کی

torque

N.m

ref

at $P_f = 0$

$$P_m = P_o + P_f$$

$$P_m = P_o = 50 \text{ hp}$$

$$= 50 \times 746 = 37300 \text{ N.m}$$

$$P_o = T_d \omega$$

$$\omega = \frac{2\pi \times 1746}{60} = 182.84$$

$$T_d = \frac{P_o}{\omega} = \frac{37300}{182.84} = 204 \text{ N.m}$$

$$T_m = 2 T_d = 408 \text{ N.m}$$

$$T_{st} = 0.4425 (204) = 90.27 \text{ N.m}$$

(3) Ratio to produce Max torque at St. to

$$R_{st} = \frac{S_2 S_1 R_2}{S_1} = \frac{1 - 0.112 (0.1)}{0.112} = 0.793$$